

OUR VINE

ANARCHY

PAGE NO. 15
MARCH

* Condition for reciprocity

The given

$$V_1 = AV_2 - BI_1 \quad \text{--- (1)}$$

which excitation V_1 at ip point & s.c. on op port eqn (1) we get

$$V_1 = -B\dot{I}_2 \quad V_2 = 0$$

$$\frac{\dot{I}_2}{V_1} = -\frac{1}{B}$$

which interchanging of excitation & response the voltage source V_2 is at ip port while s.c. current I_1 is obtain at ip point i.e. $V_1 = 0$.

This time the parameter eqns (1) & (2)

$$0 = AV_2 - BI_2$$

$$\& I_1 = CV_2 - DS_2$$

These eqn give

$$I_2 = \frac{AV_2}{B} \quad \& I_1 = CV_2 - ADV_2$$

$$V_2 = \frac{(B(-AD))}{B}$$

$$\frac{I_1}{V_2} = \frac{AD - BC}{B} \quad \text{--- (2)}$$

$$\frac{I_1}{V_2} = \frac{AD - BC}{B} \quad \text{--- (2)}$$

Q.6 Define Y parameters of two port network and deriving the condition for reciprocity & symmetry network.

Y Parameters (short circuit admittance parameters)

In two port network the YIP current I_1 & I_2 can be expressed in terms of iop & oip voltage as v_1 & v_2 resp.

$$[I] = [Y][V]$$

where $[Y]$ is admittance matrix

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$I_1 = Y_{11}v_1 + Y_{12}v_2$$

$$I_2 = Y_{21}v_1 + Y_{22}v_2$$

$$Y_{11} = \frac{I_1}{v_1} \Big|_{v_2=0} \quad \text{and} \quad Y_{21} = \frac{I_2}{v_1} \Big|_{v_2=0}$$

Similarly assuming iop port to short circuited i.e. $v_1=0$.

$$\therefore Y_{12} = \frac{I_1}{v_2} \Big|_{v_1=0} \quad \& \quad Y_{22} = \frac{I_2}{v_2} \Big|_{v_1=0}$$

= 2) Output is short circuited ($V_2 = 0$)

from eqn ③

$$0 = 2I_3 + 2I_2$$

$$\left\{ I_3 = -I_2 \right\}$$

$$\text{from eqn } ④ \\ 5(-I_2) + 2I_2 - 2I_1 = 0$$

$$-3I_2 - 2I_1$$

$$D = \frac{-I_1}{I_2} = 1.5$$

$$| D = 1.5 | \quad \underline{\text{Ans}}$$

from eqn ①

$$V_1 = 3I_1 - 2C - I_2$$

$$V_1 = 3I_1 + 2I_2$$

$$V_1 = 3(-1.5I_2) + 2I_2$$

$$V_1 = -4.5I_2 + 2I_2$$

$$V_1 = -2.5I_2$$

$$B = -V_1 = +2.5$$

$$I_2$$

$| B = 2.5 | \quad \underline{\text{Ans}}$

This ABCD parameters are

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 2.75 & 2.5 \\ 1.25 & 1.5 \end{bmatrix}$$

i) condition for symmetry is $A = D$.

Hence $2.075 \neq 1.5$

: Now is not symmetrical

ii) condition for reciprocity.

$$AD - BC = 1$$

$$(2.075 \times 1.5) - (2.5 \times 1.25) = 1$$

Hence now is reciprocal

Applying KCL at node 3

$$V_1 - 3(1.25(V_2) - V_2) + 3(1.25V_2) = 0 \\ 5V_1 + 0.125V_2 = 0 \\ V_1 = 2(2.5V_2) - 2V_2 = -6$$

Let output point is o.c. (π):
from eqn (3)

$$V_1 = 2V_2 \\ \frac{V_2}{V_1} = \frac{1}{2}$$

Substituting value of $\frac{V_2}{V_1}$ in eqn (2)

$$5\left[\frac{V_2}{V_1}\right] + 2(0) - 2V_1 = 0 \\ 2.5V_2 = 2V_1$$

$$\therefore C = \frac{V_1}{V_2} = \frac{2.5}{2} = 1.25$$

$$C = 1.25 \quad \text{Ans}$$

From eqn (1):

$$V_1 = 3V_2 - 2\left[\frac{V_2}{2}\right]$$


$$V_1 = 3V_2 - V_2$$

$$V_1 = 3(1.25V_2) - V_2$$

$$V_1 = 3.75V_2 - V_2$$

$$\therefore A = \frac{V_1}{V_2} = 2.75$$

$$A = 2.75 \quad \text{Ans}$$

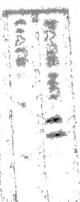

$$\beta = \frac{1}{4} L - 180^\circ$$

$$\begin{cases} C = -\frac{1}{4} \\ B = +\frac{1}{4} \end{cases}$$

To find C in complex conjugate of B .

$$C = -\frac{1}{4}$$

Substituting value of A, B, C in eqn 6.


$$I(s) = -10 \left[\frac{1}{s+5} \right] + 10 \left[\frac{1}{s+3+2j} \right] - \frac{10}{4} \left[\frac{1}{s+3-2j} \right]$$

$$I(s) = -5 \left[\frac{1}{s+5} \right] + 2.5 \left[\frac{1}{s+3+2j} \right] - 2.5 \left[\frac{1}{s+3-2j} \right]$$

Taking inverse of $I(s)$

$$i(t) = -5e^{-5t} + 2.5 e^{(3-2j)t} + 2.5 e^{(3+2j)t}$$

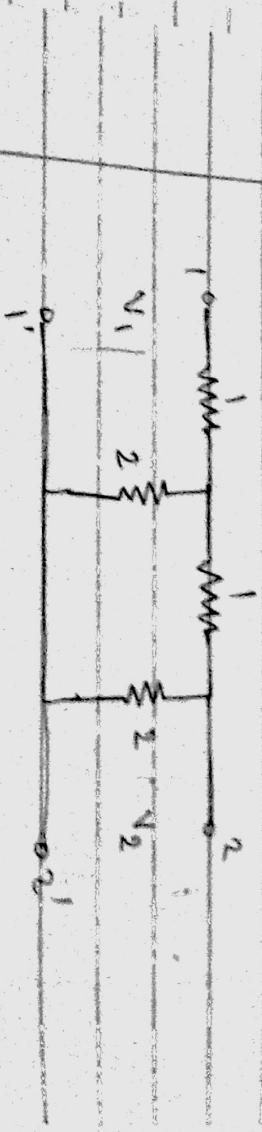- Q.7 Obtain ABCD parameters of network shown and find whether circuit is reciprocal and symmetrical.



Q.5. For the network given as $\text{I}(s)$
 $\text{I}(s) = \frac{10(s+1)}{(s+5)(s^2+6s+13)}$ place the poles
 and the zeros on s-plane and hence
 find $i(t)$

$$\text{I}(s) = \frac{10(s+1)}{(s+5)(s^2+6s+13)}$$

$$\text{I}(s) = \frac{10(s+1)}{(s+5)(s+3+2j)(s+3-2j)}$$

$$\text{Zeros} -s = -1$$

$$\text{Poles} - s = -5, s = -3+2j, -3-2j$$

By Partial fraction.

$$\text{I}(s) = \left[\frac{A}{s+5} + \frac{B}{s+3+2j} + \frac{C}{s+3-2j} \right] 10 \quad \dots \quad (1)$$

* To find A.

$$A = 4 \angle 180^\circ$$

$$\sqrt{8} L 135 \cdot \sqrt{8} L -135$$

$$\frac{4}{8} \angle 180 = -\frac{1}{2}$$

$$\therefore \boxed{A = -\frac{1}{2}}$$

* To find B

$$B = \sqrt{8} L -135$$

$$(135L)^{1/2} (4L - 90)$$

Solving eqn 1, ② ③, ④ & ⑤

$$V_3 = V_2 + I_3 s = V_2 + s V_2 s = V_2 + s^2 V \quad \text{--- (6)}$$

$$V_3 = V_2(1+s^2)$$

$$I_4 = s V_3 = s V_2(1+s^2)$$

$$I_1 = I_3 + I_4 = s V_2 + s V_2(1+s^2) \quad \text{--- (7)}$$

$$I_1 = s V_2 [1 + 1 + s^2] = s V_2 (s^2 + 2)$$

Substituting eqn ⑥ & ⑦ in eqn ⑤

$$V_1 = V_2(1+s^2) + s V_2 (s^2 + 2)s$$

$$= V_2(1+s^2) + s^2 V_2 (s^2 + 2)$$

$$V_1 = V_2 [1 + s^2 + s^4 + 2s^2]$$

$$\therefore G_{12}(s) = \frac{V_2}{V_1} = \frac{1}{s^4 + 3s^2 + 1}$$

$$Z_{12} = \frac{V_1}{I_1} = \frac{Z_{12}}{G_{12}} = \frac{V_2/I_1}{V_2/V_1} = \frac{V_1}{I_1}$$

$$Z_{12} = \frac{s^4 + 3s^2 + 1}{s^3 + 2s}$$

$$Z_{12} = \frac{V_1}{I_1} = \frac{Z_{12}}{G_{12}} = \frac{V_2/I_1}{V_2/I_1} = 1$$

$$Z_{12} = \frac{1}{s^3 + 2s}$$


$$R_2 \frac{V}{L} + L \frac{d^2 i_2(t)}{dt^2} = R_1 \left[\frac{V}{CR_1} \right]$$

$$\therefore L \frac{d^2 i_2}{dt^2} = -\frac{R_2 V}{L} + \frac{V}{CR_1}$$

$$\therefore \frac{d^2 i_2}{dt^2} = -\frac{R_2 V}{L^2} + \frac{V}{CLR_1}$$

$$\boxed{\frac{d^2 i_2}{dt^2} = \frac{V}{L} \left[\frac{1}{CR_1} - \frac{R_2}{L} \right]}$$

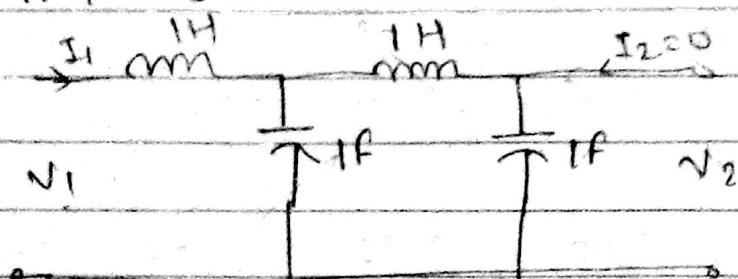
Q.4 For ladder network shown in figure
 Z_{11}, Z_{12} and G_{12} assume $I_2 = 0$:



convert in 's' domain.

From $V1\omega$
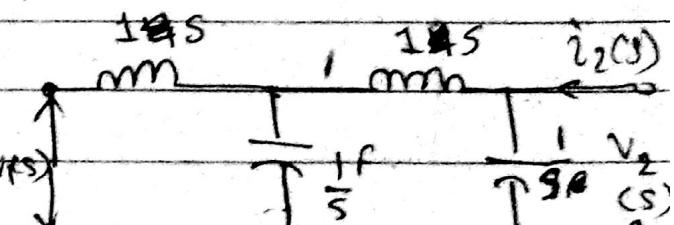
$$I_3 = \frac{V_2}{V_1} = \frac{SV_2}{V_1} \quad \text{--- (1)}$$



$$V_3 = S I_3 + V_2 \quad \text{--- (2)}$$

$$I_4 = \frac{V_3}{V_1s} = S V_3 \quad \text{--- (3)}$$

$$I_1 = I_3 + I_4 \quad \text{--- (4)}$$

$$V_1 = V_3 + I_1 s \quad \text{--- (5)}$$

Axom eqⁿ ① & ②
 $R_2 i_2(t) + L \frac{di_2}{dt} + R_1 \left[-\frac{V}{R_1} \right] = 0$

$R_2 i_2(t) + L \frac{di_2}{dt} - V = 0$

$R_2 i_2(t) + L \frac{di_2}{dt} = V$

But $i_2(t) = 0$

$\therefore L \frac{di_2}{dt} = V$

$$\boxed{\frac{di_2}{dt} = \frac{V}{L}}$$

Differentiating eqⁿ ② w.r.t 't'.

$R_2 \frac{di_2(t)}{dt} + L \frac{d^2 i_2}{dt^2} + R_1 \left[\frac{di_2(t)}{dt} - \frac{di_1(t)}{dt} \right] = 0$

Differentiating eqⁿ ③ w.r.t 't'.

$\frac{1}{C} i_1(t) + R_1 \left[\frac{di_1(t)}{dt} - \frac{di_2(t)}{dt} \right] = 0$

But $i_1(t) = \frac{V}{R_1}$


$\frac{1}{C} \frac{V}{R_1} + R_1 \left[\frac{di_1}{dt} - \frac{di_2}{dt} \right] = 0$

$$\frac{di_2}{dt} - \frac{di_1}{dt} = \frac{V}{CR_1}$$

Substitute value of $\frac{di_2}{dt}$

$$\frac{di_1}{dt} = \frac{V}{L} - \frac{V}{R_1 C}$$

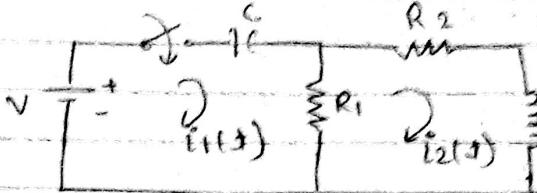Q.3 In the given network assuming all initial condition as zero, find $i_1, i_2, \frac{di_1}{dt}, \frac{di_2}{dt}, \frac{d^2i_1}{dt^2}, \text{ & } \frac{d^2i_2}{dt^2}$ at $t=0^+$



When switch is closed at $t=0$.

Apply KVL in loop 1.

$$-V + \frac{1}{C} \int i_1 dt + R_1 [i_1(t) - i_2(t)] = 0.$$

$$\therefore \frac{1}{C} \int i_1 dt + R_1 [i_1(t) - i_2(t)] = V \quad \text{--- (1)}$$

Apply KVL to loop 2

$$R_2 i_2(t) + L \frac{di_2(t)}{dt} + R_1 [i_1(t) - i_2(t)] = 0 \quad \text{--- (2)}$$


at $t=0$ capacitor \rightarrow short circuit.

Inductor $= 0$.

$$\therefore \frac{1}{C} \int i_1(t) dt = 0.$$

$$\therefore i_1(t) = 0 \quad \text{Ans.}$$

$$i_1(t) = \frac{V}{R_1}$$

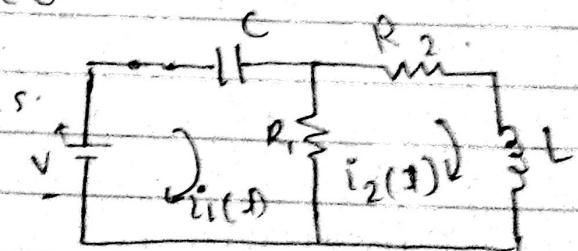

$$\text{eqn (1)} \Rightarrow 0 + R_1 [i_1(t) - i_2(t)] = V.$$

$$i_1(t) - i_2(t) = \frac{V}{R_1} \quad \text{--- (3)}$$

Differentiate eqn ① w.r.t. 'A'

$$0 = R_1 \left[\frac{di}{dt} - \frac{V_o}{L} \right] + \frac{1}{c} (i_1 - i)$$

$$0 = R_1 \left[\frac{di}{dt} - \frac{V_o}{L} \right] + \frac{1}{c} \left[\frac{V_o}{R_1} - 0 \right]$$

$$R_1 \frac{di}{dt} = \frac{V_o R_1}{L} - \frac{V_o}{R_1 c} = V_o \left[\frac{R_1}{L} - \frac{1}{R_1 c} \right]$$

$$\therefore \frac{di}{dt} = \frac{V_o}{L} - \frac{V_o}{R_1 c}$$

Differentiate eqn ② w.r.t. 'A'

$$0 = L \frac{d^2 i}{dt^2} + R_2 \frac{di}{dt} + \frac{1}{c} (i - i_1) + R_1 \left[\frac{di}{dt} - \frac{V_o}{L} \right]$$

$$0 = L \frac{d^2 i}{dt^2} + R_2 \frac{V_o}{L} + \frac{1}{c} \left(0 - \frac{V_o}{R_1} \right) + R_1 \left[\frac{V_o}{L} - \frac{V_o}{L} + \frac{V_o}{R_1 c} \right]$$

$$0 = L \frac{d^2 i}{dt^2} + \frac{R_2 V_o}{L} - \frac{V_o}{R_1 c} + \frac{V_o}{R_1 c}$$

$$L \frac{d^2 i}{dt^2} + \frac{R_2 V_o}{L}$$

$$\boxed{\frac{d^2 i}{dt^2} = - \frac{R_2 V_o}{L^2}} \Rightarrow \underline{\text{Ans}}$$

2) When switch is closed at $t=0$:

Apply KVL to loop 1

$$V_0 = R_1(i_1 - i) + \frac{1}{C} \int (i_1 - i) dt$$

\square Apply KVL to loop 2

$$0 = L \frac{di}{dt} + R_2 i + \frac{1}{C} \int (i - i_1) dt + R_1(i - i_1)$$

$$\frac{di}{dt} = 0^+ \quad \text{At } t = 0^+$$

capacitor acts as short \rightarrow induction open circuit

$$\therefore \frac{1}{C} \int i_1 - i = \frac{1}{C} \int i - i_1 = 0$$

Similarly current through L is zero

$$\therefore i = 0$$

$$\therefore \textcircled{1} \Rightarrow V_0 = R_1(i_1 - 0) + 0$$

$$\boxed{i_1 = \frac{V_0}{R_1}}$$

From \textcircled{2}

$$L \frac{di}{dt} + R_2(0) + 0 + R_1(0 - \frac{V_0}{R_1}) = 0$$


$$L \frac{di}{dt} - V_0 = 0$$

$$\boxed{\frac{di}{dt} = \frac{V_0}{L}} \Rightarrow \text{Ans.}$$

$$(40 + 6s) I(s) = 12$$

$$I(s) = \frac{12}{6s + 40} = \frac{12}{s + 40/6} = \frac{12}{s + 2}$$


$$= \frac{2}{s + 40/6}$$

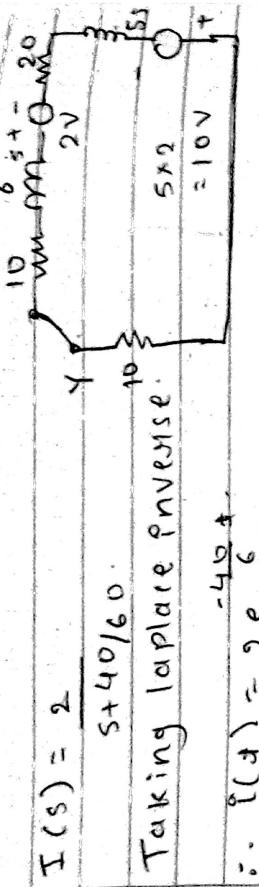


Taking Laplace inverse.

$$\therefore i(t) = 2e^{-4t}$$

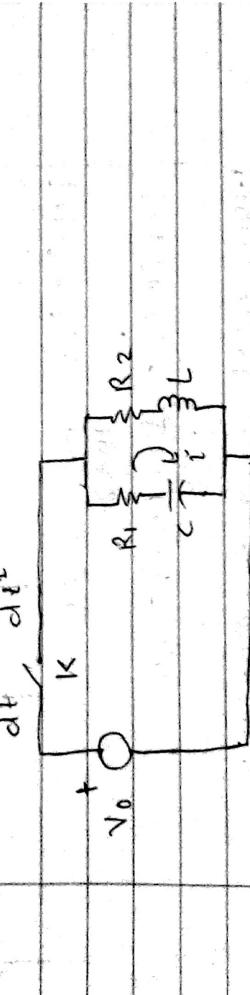Q.2 From the network shown in Fig. 3 switch K is closed at instant $t=0$, connecting the battery to an unenergised network. Find $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t=0^+$



- 1) When switch is opened

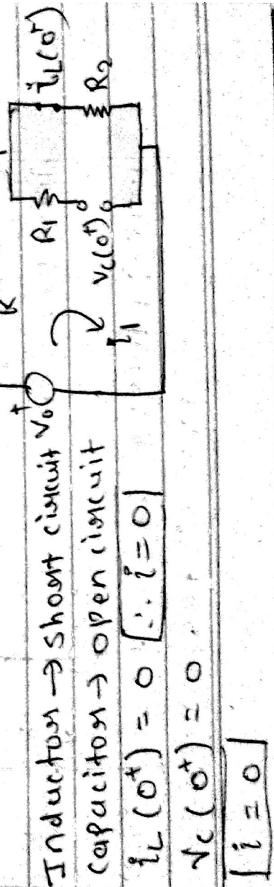

$$i_L(0^+) = 0 \quad (\because i = 0)$$

$$V_C(0^+) = 0 \quad (\because i = 0)$$

$$i = 0$$


Assignment NO-2

Shruti Ghodke Roll no-
Section -B B-15

Page No. /


Date:

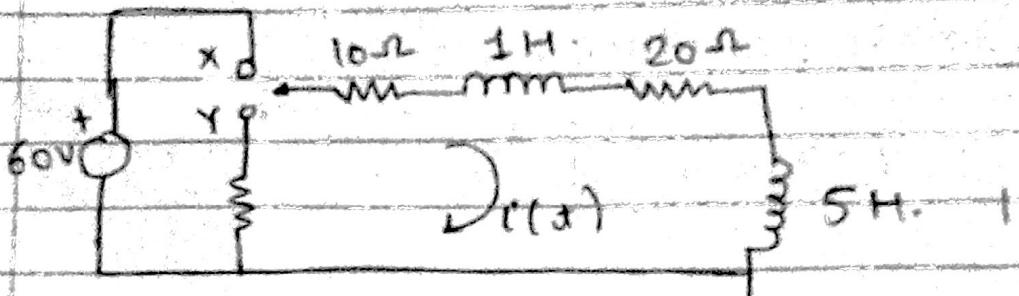- Q.1** For the network shown, find Particular solution for $i(t)$ when switch K is moved from position X to Y at time $t=0$, and the steady state current having previously established in the circuit.



When switch is at 'X'
(steady state cond.)

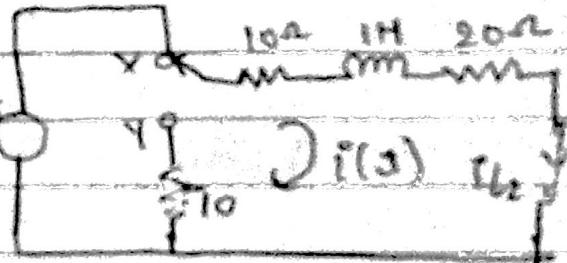Inductor acts as a s.c
 $\therefore i_L(0^+)$



$$i_L(0^+) = I_{L_2}(0^+) = \frac{60}{10+20} = \frac{60}{30} = 2A$$

$$i_L(0^+) = I_{L_2}(0^+) = 2A$$

When switch is at Position 'Y':-

→ converting the above network into 's' domain:

Apply KVl to loop

$$10I(s) + 10(s) + 5I(s)$$

$$- 2 + 20I(s) + 5sI(s) - 10 = 0$$

